

NAME - ARIJIT GHOSAL

STREAM- INFORMATION TECHNOLOGY

MAKAUT ROLL NO- 11200221003

SUBJECT- ANALOG & DIGITAL ELECTRONICS LAB

**COLLEGE- GOVERNMENT COLLEGE OF
ENGINEERING AND LEATHER TECHNOLOGY**

SEMESTER- 3RD

SESSION- 2022-23

EXPERIMENT NO. 4


Design a 2-to-4 Line Decoder with Enable input using minimum number of basic gates.

TRUTH TABLE


E_n	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

PIN DIAGRAM OF THE ICs USED


1) AND GATE

 


2) NOT GATE

 

CIRCUIT DIAGRAM

 

CONCLUSION

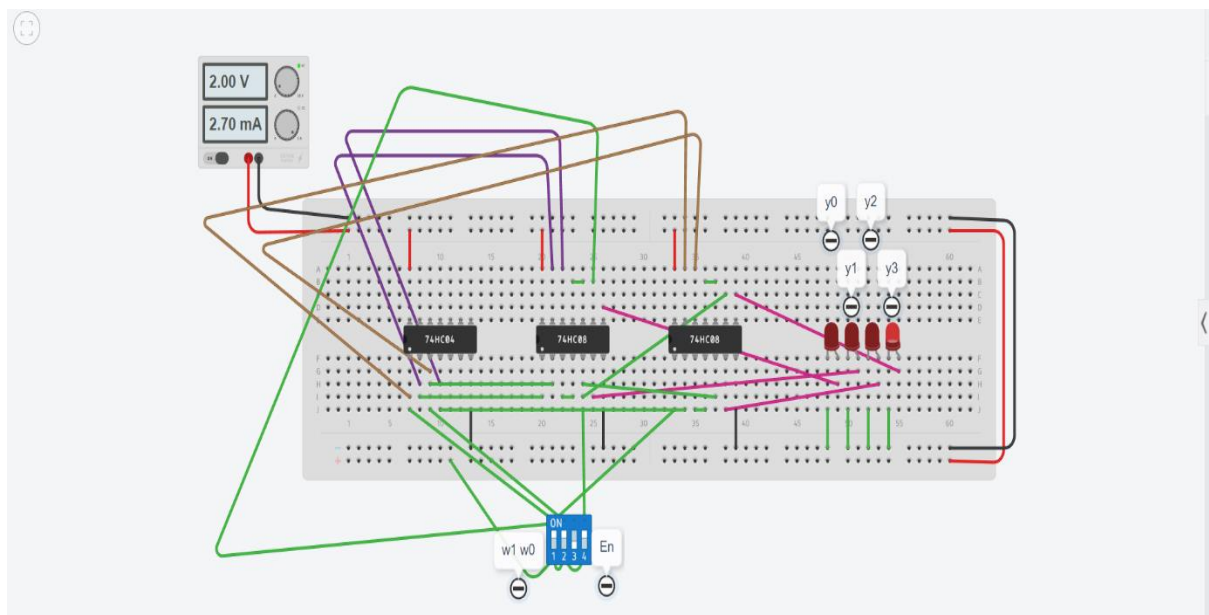

EXPERIMENT NO. 5


Design a MODULO-4 Asynchronous up Counter (MOD-4 UP RIPPLE Counter).

COUNTER STATE TABLE


Counter State	Q1	Q0
0	0	0
1	0	1
2	1	0
3	1	1
0	0	0

PIN DIAGRAM OF THE ICs USED


1) JK Flip Flop

 


CIRCUIT DIAGRAM

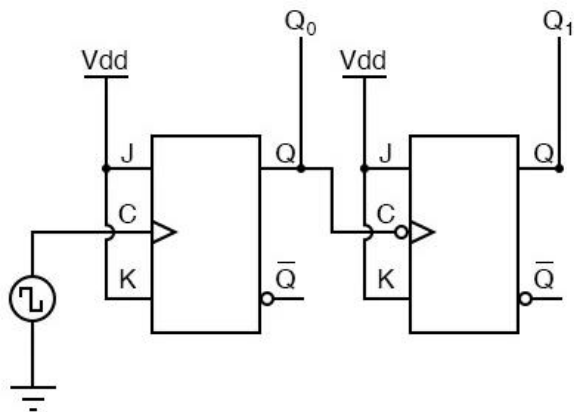

TIMING DIAGRAM

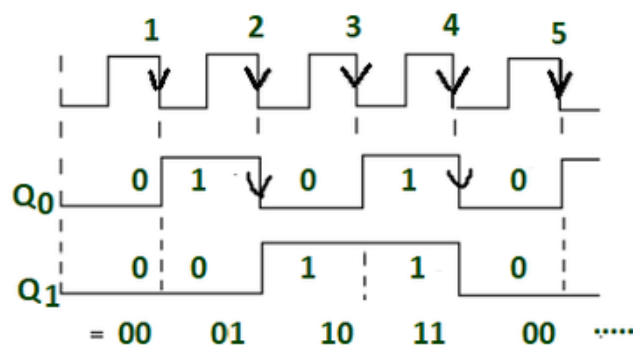


CONCLUSION

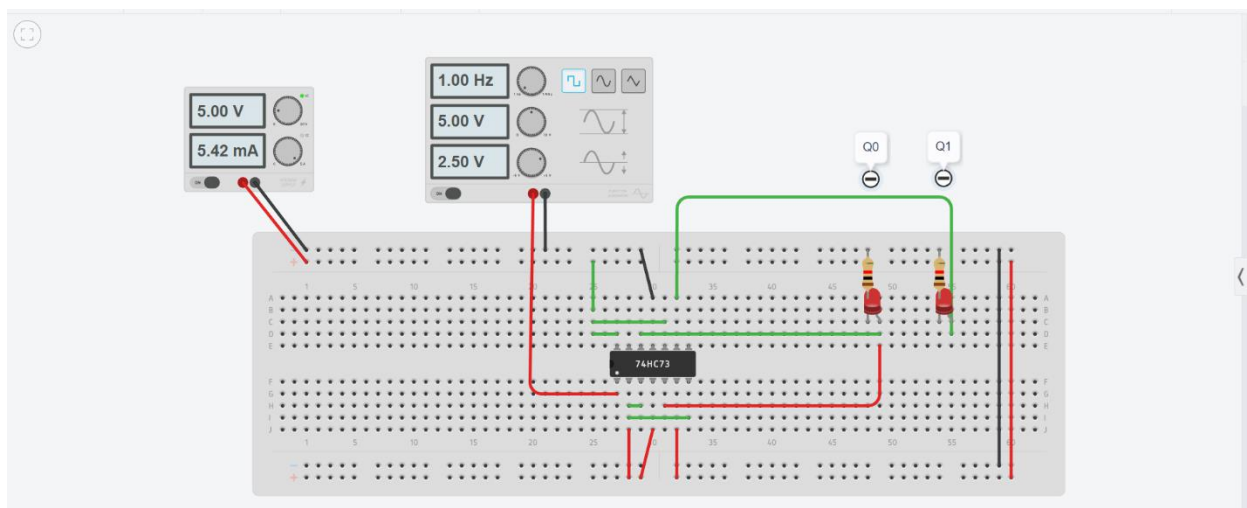

EXPERIMENT NO. 6

Design a MODULO-3 Synchronous up Counter.

Pin Diagram of JK Flip Flop (7473 IC)

 

Counter State Table

Present State		Next State		Inputs			
Q ₁	Q ₀	Q ₁	Q ₀	J ₁	K ₁	J ₀	K ₀
0	0	0	1	0	x	1	x
0	1	1	0	1	x	x	1
1	0	0	0	x	1	0	x

Boolean Expression and K-map

$Q_1 \backslash Q_0$	Q_0'	Q_0
Q_1'	0	1
Q_1	x	x

$$J_1 = Q_0$$

$Q_1 \backslash Q_0$	Q_0'	Q_0
Q_1'	1	x
Q_1	0	x

$$J_0 = Q_1'$$

$Q_1 \backslash Q_0$	Q_0'	Q_0
Q_1'	x	x
Q_1	1	x


$$K_1 = 1$$

$Q_1 \backslash Q_0$	Q_0'	Q_0
Q_1'	x	1
Q_1	x	x

$$K_0 = 1$$

Circuit Diagram and Timing Diagram

8.3 Synchronous Counters (cont.)

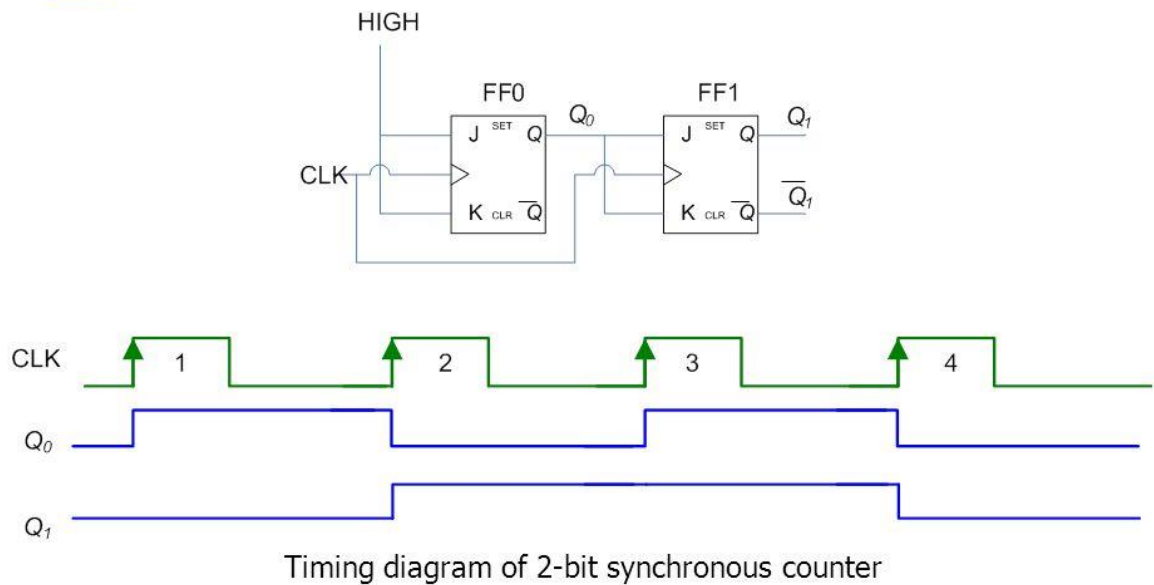

241-208 CH8

13

CONCLUSION

